 


separate column for each binary bit. Inside this spreadsheet, create a new column for the N control signals needed by your datapath implementation. The end result should be an $N \times M$ table where each row corresponds to the output of the control logic module for a given instruction.

	A	B	C	D	E	F	G	H	I	J	K	L	M	N
1	Instruction	Opcode (Binary)	Funct (Binary)	ALUSrc	ALUOp	ALUControl	MemtoReg	MemRead	MemWr	RegWr	RegDst	Jump	Branch	Type
3	add	"000000"	"100000"	0	"10"	"0010"	0	0	0	1	1 [rd]	0	0	R
4	addu	"000000"	"100001"	0	"10"	"0010"	0	0	0	1	1	0	0	R
5	and	"000000"	"100100"	0	"10"	"0000"	0	0	0	1	1	0	0	R
6	nor	"000000"	"100111"	0	"10"	"0101"	0	0	0	1	1	0	0	R
7	xor	"000000"	"100110"	0	"10"	"0011"	0	0	0	1	1	0	0	R
8	or	"000000"	"100101"	0	"10"	"0001"	0	0	0	1	1	0	0	R
9	slt	"000000"	"101010"	0	"10"	"0111"	0	0	0	1	1	0	0	R
10	sll	"000000"	"000000"	0	"10"	"0100"	0	0	0	1	1	0	0	R
11	srl	"000000"	"000010"	0	"10"	"0100"	0	0	0	1	1	0	0	R
12	sra	"000000"	"000011"	0	"10"	"0100"	0	0	0	1	1	0	0	R
13	sub	"000000"	"100010"	0	"10"	"0110"	0	0	0	1	1	0	0	R
14	subu	"000000"	"100011"	0	"10"	"0110"	0	0	0	1	1	0	0	R
15	jr	"000000"	"001000"	x/0	"10"	"0010"	0	0	0	1	x/1	0	0	R
16	sliv	"000000"	"000100"	0	"10"	"0100"	0	0	0	1	x/1	0	0	R
17	srlv	"000000"	"000110"	0	"10"	"0100"	0	0	0	1	x/1	0	0	R
18	sra	"000000"	"000111"	0	"10"	"0100"	0	0	0	1	x/1	0	0	R
19	beq	"000100"	"-----"	x/1	"01"	"0110"	x/0	0	0	0	x	0	1	I
20	bne	"000101"	"-----"	x/1	"01"	"0110"	0	0	0	0	x	0	1	I
21	addi	"001000"	"-----"	1	"00"	"0010"	0	0	0	1	0 [rt]	0	0	I
22	addiu	"001001"	"-----"	1	"00"	"0010"	0	0	0	1	0	0	0	I
23	slti	"001010"	"-----"	1	"00"	"0111"	0	0	0	1	0	0	0	I

Attached .xls in zip submission.

[Part 2 (a.ii)] Implement the control logic module using whatever method and coding style you prefer. Create a testbench to test this module individually and show that your output matches the expected control signals from problem 1(a).



The above waveforms demonstrate that the control logic is working correctly. Since the waveforms are a little trickier to follow, we used asserts, which we'll discuss below. In the waveform diagram above, we can see that the first 13 tests are R-type instructions with all 0 opcodes. The ALUOp output was correct for all of them.

We came across asserts in VHDL, and they have made writing and checking tests a lot easier. Here is an example of a test with an assert:

```

98      s_opCode <= "000000";
99      s_funcCode <= "100000";
100     WAIT FOR CLOCK_PERIOD; --add instruction
101     ASSERT s_ALUOp = b"0010" REPORT "Wrong ALUOp" SEVERITY error;

```

We checked to ensure the ALUOp output was correct because that is what changes based on the opcode and functcode. We have a total of 27 tests, and each of them is written like the one above.

Instance	Design unit	Design unit type	Top Category	Visibility	Total coverage	Assertions count	Assertions hit	Assertions missed	Assertion %	Assertion graph
tb_control	tb_control(struct...	Architecture	DU Instance	+acc=<fu...	100.00%	27	27	0	100.00%	
DUT0	control(behavior...	Architecture	DU Instance	+acc=<fu...						
TEST_CASES	tb_control(struct...	Process	-	+acc=<fu...						
standard	standard	Package	Package	+acc=<fu...						
textio	textio	Package	Package	+acc=<fu...						
std_logic_1164	std_logic_1164	Package	Package	+acc=<fu...						
std_logic_textio	std_logic_textio	Package	Package	+acc=<fu...						


This picture shows that all the assertions hit.

[Part 2 (b.i)] What are the control flow possibilities that your instruction fetch logic must support? Describe these possibilities as a function of the different control flow-related instructions you are required to implement.

The instruction fetch logic must support various control flow possibilities based on the different control flow-related instructions required to implement. These possibilities can be described as follows:

1. **Non-Control Flow:** In this scenario, the program counter (PC) is incremented by 4, indicating sequential execution of instructions.
2. **Jump (j):** The PC is set to the value specified by JumpAddr, which is calculated as $\{ PC+4[31:28], \text{address}, 2'b0 \}$.
3. **Jump Register (jr):** The PC is set to the value stored in register R[rs].
4. **Jump and Link (jal):** This instruction involves two steps:
R[31] is set to $PC + 8$.
PC is set to the value specified by JumpAddr.
5. **Branch on Equal (beq):** If the contents of registers R[rs] and R[rt] are equal, the PC is updated using the formula $PC = PC + 4 + \text{BranchAddr}$.
6. **Branch Not Equal (bne):** If the contents of registers R[rs] and R[rt] are not equal, the PC is updated using the formula $PC = PC + 4 + \text{BranchAddr}$.

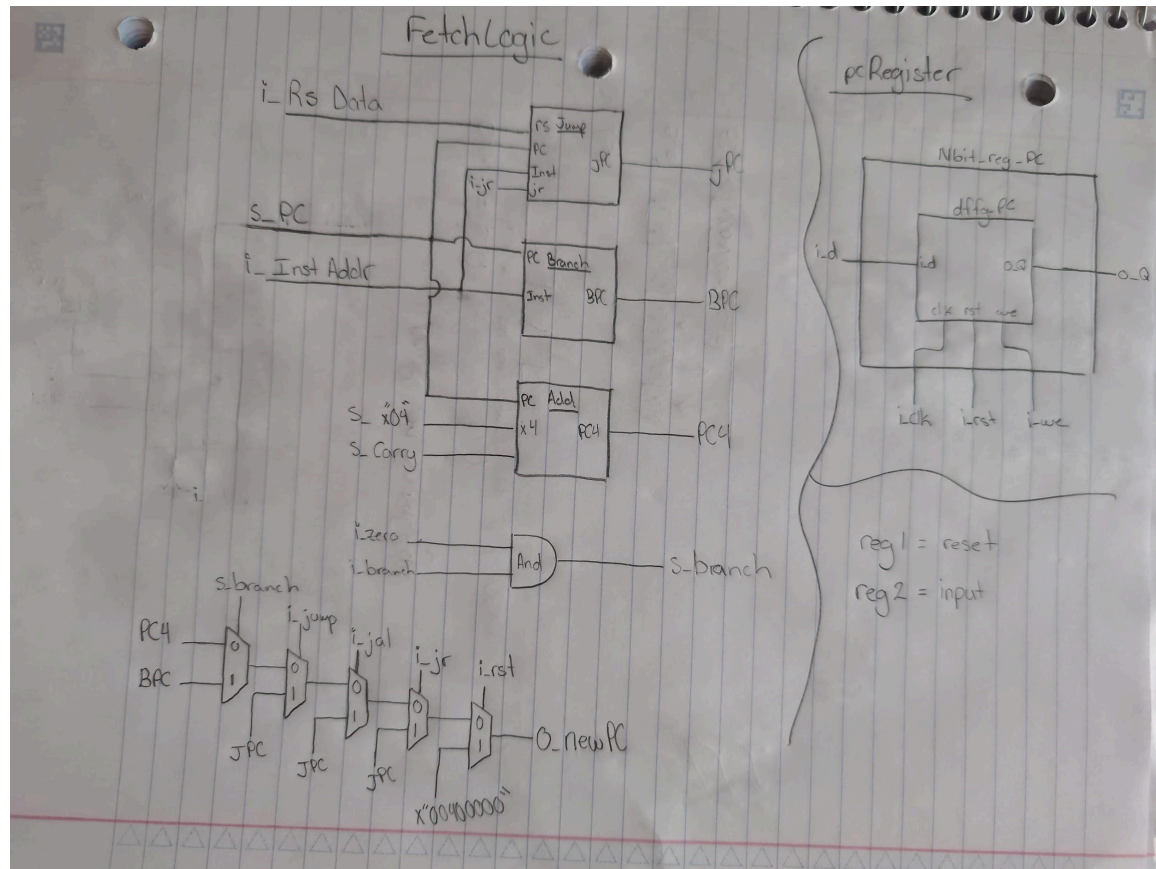[Part 2 (b.ii)] Draw a schematic for the instruction fetch logic and any other datapath modifications needed for control flow instructions. What additional control signals are needed?



[Part 2 (b.iii)] Implement your new instruction fetch logic using VHDL. Use QuestaSim to test your design thoroughly to make sure it is working as expected. Describe how the execution of the control flow possibilities corresponds to the QuestaSim waveforms in your writeup.

[Part 2 (c.i.1)] Describe the difference between logical (srl) and arithmetic (sra) shifts. Why does MIPS not have a sla instruction?

The distinction between logical (SRL) and arithmetic (SRA) shifts lies in how they handle shifting operations, particularly with signed values.

Shift Right Logical (SRL): This operation shifts the bits of a value to the right, filling the vacant leftmost bits with zeros. While this is straightforward and efficient for unsigned values, it can lead to unexpected results with signed values. This is because the insertion of zeros doesn't consider the sign of the value, potentially altering the sign bit and causing unexpected behavior.

Shift Right Arithmetic (SRA): Unlike SRL, SRA takes into account the sign of the value being shifted. It shifts the bits to the right but fills the vacant leftmost bits with

copies of the sign bit, maintaining the sign and ensuring predictable results, especially with signed values.

MIPS doesn't have a SLA (Shift Left Arithmetic) instruction because SLA could lead to unpredictable outcomes, particularly with signed values. SLA would insert the sign bit into the least significant bit position when shifting left. However, since the most significant bit would eventually be shifted out, the result could flip from positive to negative or vice versa, depending on the current MSB and the number of shifts. This unpredictability makes SLA less useful and potentially problematic for maintaining the integrity of signed values during shifting operations. Therefore, MIPS architecture opts not to include an SLA instruction to avoid such issues.

[Part 2 (c.i.2)] In your writeup, briefly describe how your VHDL code implements both the arithmetic and logical shifting operations.

[Part 2 (c.i.3)] In your writeup, explain how the right barrel shifter above can be enhanced to also support left shifting operations.

[Part 2 (c.i.4)] Describe how the execution of the different shifting operations corresponds to the QuestaSim waveforms in your writeup.

[Part 2 (c.ii.1)] In your writeup, briefly describe your design approach, including any resources you used to choose or implement the design. Include at least one design decision you had to make.

[Part 2 (c.ii.2)] Describe how the execution of the different operations corresponds to the QuestaSim waveforms in your writeup.

[Part 2 (c.iii)] Draw a simplified, high-level schematic for the 32-bit ALU. Consider the following questions: how is Overflow calculated? How is Zero calculated? How is `slt` implemented?

[Part 2 (c.v)] Describe how the execution of the different operations corresponds to the QuestaSim waveforms in your writeup.

[Part 2 (c.viii)] justify why your test plan is comprehensive. **Include waveforms** that demonstrate your test programs functioning.

[Part 3] In your writeup, show the QuestaSim output for each of the following tests, and provide a discussion of result correctness. It may be helpful to also annotate the waveforms directly.

[Part 3 (a)] Create a test application that makes use of every required arithmetic/logical instruction at least once. The application need not perform any particularly useful task, but it should demonstrate the full functionality of the processor (e.g., sequences of many instructions executed sequentially, 1 per cycle while data written into registers can be effectively retrieved and used by later instructions). Name this file Proj1_base_test.s.

[Part 3 (b)] Create and test an application which uses each of the required control-flow instructions and has a call depth of at least 5 (i.e., the number of activation records on the stack is at least 4). Name this file Proj1_cf_test.s.

[Part 3 (c)] Create and test an application that sorts an array with N elements using the BubbleSort algorithm ([link](#)). Name this file Proj1_bubblesort.s.

[Part 4] Report the maximum frequency your processor can run at and determine what your critical path is. Draw this critical path on top of your top-level schematic from part 1. What components would you focus on to improve the frequency?

FMax: 22.54mhz Clk Constraint: 20.00ns Slack: -24.37ns

The path is given below

```
=====
From Node      : pcRegister:PC_REG|Nbit_reg_PC:REG|dffg_PC:\G_NBit_Reg:9:REG|s_Q
To Node       : MIPSregister:G_REG|Nbit_reg:\regi:21:REG|dffg:\G_NBit_Reg:20:REG|s_Q
Launch Clock  : iCLK
Latch Clock   : iCLK
Data Arrival Path:
Total (ns)    Incr (ns)    Type    Element
=====
0.000         0.000        launch edge time
3.091         3.091    R      clock network delay
3.323         0.232    uTco   pcRegister:PC_REG|Nbit_reg_PC:REG|dffg_PC:\G_NBit_Reg:9:REG|s_Q
3.323         0.000    FF    CELL PC_REG|REG|\G_NBit_Reg:9:REG|s_Q|q
4.692         1.369    FF    IC   s_IMemAddr[9]~4|datad
4.817         0.125    FF    CELL s_IMemAddr[9]~4|combout
7.815         2.998    FF    IC   IMem|ram~45332|dataa
8.239         0.424    FF    CELL IMem|ram~45332|combout
8.506         0.267    FF    IC   IMem|ram~45333|datab
8.931         0.425    FF    CELL IMem|ram~45333|combout
10.628        1.697    FF    IC   IMem|ram~45336|datad
10.753        0.125    FF    CELL IMem|ram~45336|combout
10.980        0.227    FF    IC   IMem|ram~45339|datad
11.105        0.125    FF    CELL IMem|ram~45339|combout
11.332        0.227    FF    IC   IMem|ram~45340|datad
11.457        0.125    FF    CELL IMem|ram~45340|combout
13.219        1.762    FF    IC   IMem|ram~45383|datac
13.500        0.281    FF    CELL IMem|ram~45383|combout
13.767        0.267    FF    IC   IMem|ram~45426|datab
14.171        0.404    FF    CELL IMem|ram~45426|combout
14.406        0.235    FF    IC   IMem|ram~45597|datac
14.687        0.281    FF    CELL IMem|ram~45597|combout
14.912        0.225    FF    IC   IMem|ram~45768|datad
15.062        0.150    FR    CELL IMem|ram~45768|combout
15.753        0.691    RR    IC   G_REG|mux2|mx_out[10]~20|datad
15.908        0.155    RR    CELL G_REG|mux2|mx_out[10]~20|combout
16.680        0.772    RR    IC   G_REG|mux2|mx_out[2]~548|datad
16.835        0.155    RR    CELL G_REG|mux2|mx_out[2]~548|combout
19.671        2.836    RR    IC   G_REG|mux2|mx_out[2]~549|datad
19.826        0.155    RR    CELL G_REG|mux2|mx_out[2]~549|combout
20.033        0.207    RR    IC   G_REG|mux2|mx_out[2]~553|datad
20.188        0.155    RR    CELL G_REG|mux2|mx_out[2]~553|combout
20.390        0.202    RR    IC   G_REG|mux2|mx_out[2]~556|datad
20.545        0.155    RR    CELL G_REG|mux2|mx_out[2]~556|combout
21.514        0.969    RR    IC   G_ALU|G_MUX_IMM|\G_NBit_MUX:2:MUXI|o_0~0|datad
21.669        0.155    RR    CELL G_ALU|G_MUX_IMM|\G_NBit_MUX:2:MUXI|o_0~0|combout
=====
```


21.669	0.155	RR	CELL	G_ALU G_MUX_IMM G_NBit_MUX:2:MUXI o_0~0 combout
22.129	0.460	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:2:ADDI1 OR1 o_F~0 datad
22.284	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:2:ADDI1 OR1 o_F~0 combout
22.512	0.228	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:3:ADDI1 OR1 o_F~0 datad
22.667	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:3:ADDI1 OR1 o_F~0 combout
22.894	0.227	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:4:ADDI1 OR1 o_F~0 datad
23.049	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:4:ADDI1 OR1 o_F~0 combout
23.277	0.228	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:5:ADDI1 OR1 o_F~0 datad
23.432	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:5:ADDI1 OR1 o_F~0 combout
23.660	0.228	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:6:ADDI1 OR1 o_F~0 datad
23.815	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:6:ADDI1 OR1 o_F~0 combout
24.029	0.214	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:7:ADDI1 OR1 o_F~0 datad
24.184	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:7:ADDI1 OR1 o_F~0 combout
24.881	0.697	RR	IC	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:8:ADDI1 XOR2 o_F datad
25.036	0.155	RR	CELL	G_ALU G_ADDSUB N_Bit_Adder G_NBit_Adder:8:ADDI1 XOR2 o_F combout
25.240	0.204	RR	IC	G_ALU G_SELECT o_result[8]~116 datad
25.395	0.155	RR	CELL	G_ALU G_SELECT o_result[8]~116 combout
25.598	0.203	RR	IC	G_ALU G_SELECT o_result[8]~117 datad
25.753	0.155	RR	CELL	G_ALU G_SELECT o_result[8]~117 combout
26.440	0.687	RR	IC	G_ALU G_SELECT o_result[8]~119 datad
26.727	0.287	RR	CELL	G_ALU G_SELECT o_result[8]~119 combout
26.930	0.203	RR	IC	G_ALU G_SELECT o_result[8]~230 datad
27.085	0.155	RR	CELL	G_ALU G_SELECT o_result[8]~230 combout
29.262	2.177	RR	IC	DMem ram~37013 dataa
29.659	0.397	RR	CELL	DMem ram~37013 combout
40.492	10.833	RR	IC	DMem ram~37014 datad
40.779	0.287	RR	CELL	DMem ram~37014 combout
40.983	0.204	RR	IC	DMem ram~37015 datad
41.138	0.155	RR	CELL	DMem ram~37015 combout
41.341	0.203	RR	IC	DMem ram~37026 datad
41.496	0.155	RR	CELL	DMem ram~37026 combout
42.209	0.713	RR	IC	DMem ram~37027 datad
42.496	0.287	RR	CELL	DMem ram~37027 combout
42.703	0.207	RR	IC	DMem ram~37070 datad
42.842	0.139	RR	CELL	DMem ram~37070 combout
43.117	0.275	FF	IC	DMem ram~37582 dataa
43.541	0.424	FF	CELL	DMem ram~37582 combout
43.950	0.409	FF	IC	G_MUX_JAL G_NBit_MUX:20:MUXI o_0~0 datad
44.075	0.125	FF	CELL	G_MUX_JAL G_NBit_MUX:20:MUXI o_0~0 combout
44.302	0.227	FF	IC	G_MUX_JAL G_NBit_MUX:20:MUXI o_0~1 datad
44.427	0.125	FF	CELL	G_MUX_JAL G_NBit_MUX:20:MUXI o_0~1 combout
47.406	2.979	FF	IC	G_REG regi:21:REG G_NBit_Reg:20:REG s_Q asdata
47.807	0.401	FF	CELL	MIPSregister:G_REG Nbit_reg:regi:21:REG dffg:G_NBit_Reg:20:REG s_Q

Data Required Path:

Total (ns)	Incr (ns)	Type	Element
20.000	20.000		latch edge time
23.430	3.430	R	clock network delay
23.438	0.008		clock pessimism removed
23.418	-0.020		clock uncertainty
23.436	0.018	uTsu	MIPSregister:G_REG Nbit_reg:regi:21:REG dffg:G_NBit_Reg:20:REG s_Q
Data Arrival Time : 47.807			
Data Required Time : 23.436			
Slack : -24.371 (VIOLATED)			